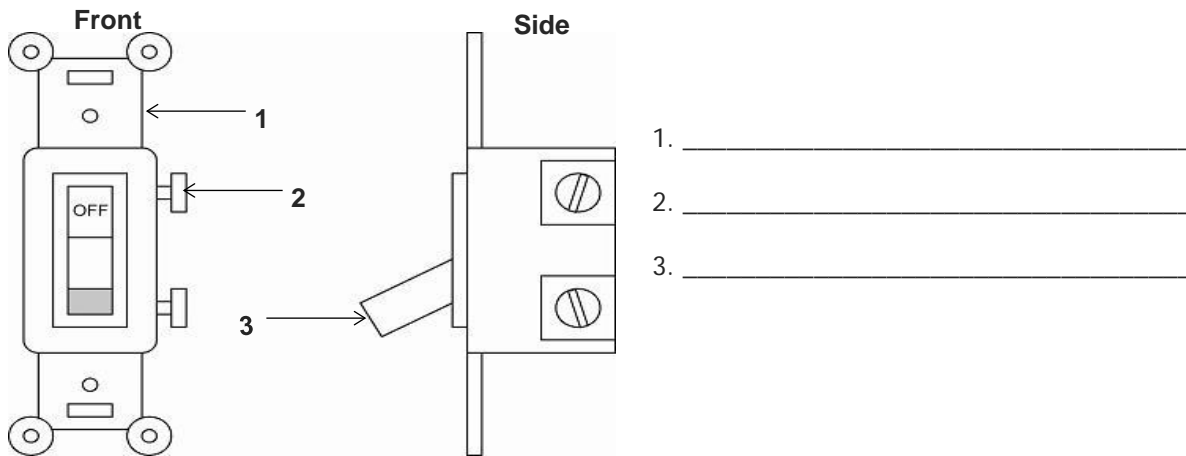


Electrical Switch Quiz

Direction: Name the parts of the switch below and the questions that follow using the History of Switches.

Use complete sentences when answering the questions.



4. What is the wire that carries the current often called?

- A. hot B. neutral C. cold
-

5. What is the purpose of a three-way light switch?

- A. It allows you to dim the light.
 - B. It allows you to control the light from two switches.
 - C. It allows one light switch to control three different lights.
-

6. Why can't you mark the on and off positions on a three-way switch?

- A. both positions can turn the light on and off.
 - B. The switch is inaccessible.
 - C. It is important for the electrician to figure it out by himself.
-

7. How many switches do you need to construct a three-way switch circuit?

- A. 1 B. 2 C. 3
-